

Faculty of Engineering & Technology

Electrical & Computer Engineering Department

Advanced Digital – ENCS3310

Project Report – Design Of Multi-Cycle Processor

Prepared by:

Name: Raghad Jamhour.

Number: 1220212.

Name: Rawaa Hammad.

Number: 1210927.

Instructor: Ayman Hroub.

Date: 20/08/2024.

Abstract

This project involves the development of a multi-cycle processor in advanced digital design. The used components are 16-bit ALU, Register File with 16 general-purpose registers each 16 bits wide, Data memory and an instruction memory along with a control unit. The processor executes 16-bit machine instructions across five stages: fetch, decode, execute, memory, and write-back. The ALU performs arithmetic and logical operations using a 4-bit opcode, while the Register File provides fast data access. This project offers efficient instruction execution through clock cycles and proper control signal generation. Testing is performed to verify that the processor correctly handles R-type and M-type. It focuses on ensuring proper transitions between different stages and overall processor functionality. The results and simulations, are presented to show how the processor performs.

Table of Contents

Abstract.....	2
Table of figures	4
List of tables	5
Brief introduction and background	5
1- Arithmetic Logic Unit (ALU).....	5
2- Register File.....	5
3- Data Memory	5
4- Instruction Memory	6
5- Control Unit.....	6
Design Philosophy	7
• MCP Philosophy	7
Inputs and Outputs	7
States.....	7
State Transitions.....	7
Test cases and Simulation results.....	14
Conclusion and future work.....	17

Table of figures

Figure 1: Design.....	13
Figure 2: Test Bench	14
Figure 3: Results	15

List of tables

Table 1 : Opcode's operations.	7
--------------------------------	---

Brief introduction and background

1- Arithmetic Logic Unit (ALU)

In our multi-cycle processor, the ALU (Arithmetic Logic Unit) is a crucial component that performs arithmetic and logic operations. The ALU processes two 16-bit inputs. Based on a 4-bit opcode sent by the control unit, the ALU can execute various operations including addition, subtraction, bitwise AND, OR, and XOR and the result is the output of the ALU. This design allows for efficient execution of R-Type instructions, ensuring accurate operations within the processor.

2- Register File

The register file is a vital component of the processor since it temporarily stores data during transfers between memory and operational units. The processor accesses this data using two registers, Rs1 and Rs2. Data from Rs1 is accessed using the input address (read_port1 in our design) and the value is assigned to readData1, while data from Rs2 is accessed using the second input address (read_port2 in our design) is assigned to readData2. The register Rd is the destination for writing data, when the control signal writeEn is 1, Rd is accessed using the input address (write_port) then the data on writeData is written into Rd.

3- Data Memory

In our processor, the memory is divided into two separate sections: Instruction Memory and Data Memory. This division helps avoid conflicts that could occur when fetching instructions while simultaneously loading or storing data.

The data memory is connected to the datapath through an address input and two data lines: one as an output for the data and the other is an input for writing on the memory. When the MemRd signal is set to 1, the data memory gets the data stored in the specified address and outputs it. When the MemWrite signal is set to 1, it writes the input data to the specified address.

4- Instruction Memory

The instruction memory is designed to store instructions and is designed only for reading, taking a 16-bit address from the Program Counter (PC) only 8 is used of it in our design since the memory is 512 bytes (256 addresses * 2 Bytes), then providing a corresponding 16-bit instruction.

5- Control Unit

The control unit in our processor is responsible for generating control signals based on the instruction's opcode. It takes the 4-bit opcode and produces appropriate control signals for the operations. The control unit outputs signals for register writing (RegWr), memory reading (MemRd), memory writing (MemWr), and ALU operation (ALUop). The logic is implemented using a combinational always block with a case statement to set these signals according to the opcode received. This ensures that the processor correctly performs arithmetic, logical, load, and store operations by managing the flow of data through the instruction stages.

Design Philosophy

• MCP Philosophy

Inputs and Outputs

The module receives a clock signal (clk) and a reset signal (reset). The operation of the microprocessor occurs at the rising edge of the clk, while the reset signal resets the system to the fetch stage.

On the other hand the module outputs multiple signals:

- ✚ current_state and next_state: These indicate the current and upcoming states of the microprocessor.
- ✚ PC (Program Counter): Saves the address of the next instruction to be executed.
- ✚ IR (Instruction Register): Holds the current instruction being executed.
- ✚ ALUresult: Stores the result of operations performed by the ALU.
- ✚ memData: Holds data read from memory.
- ✚ writeData: Holds data that will be written back to a register.

States

The microprocessor operates through a finite state machine (FSM) with the following states:

1. **FETCH (000)**: The microprocessor fetches the next instruction from memory using the PC and stores it in the IR.
2. **DECODE (001)**: The instruction in IR is decoded to determine the operation to be performed and the registers involved, it takes the first 4 bits as the Rs2 and the next 4 as Rs1 then another 4 as the Rd and finally the last 4 are the OpCode.
3. **EXECUTE (010)**: The operation specified by the instruction is getting executed in this stage, such as arithmetic operations performed by the ALU which are specified in table1 below.
4. **MEM_ACCESS (011)**: If the instruction involves reading from or writing to memory, this state handles the memory operations.
5. **WRITE_BACK (100)**: The result of the operation (either from the ALU or memory) is written back to the destination register.

State Transitions

- ✚ The microprocessor starts in the FETCH state, where it loads the next instruction.
- ✚ It then moves to the DECODE state to specify what the instruction does.
- ✚ If the instruction is an R-type it will move to EXECUTE to perform an operation and if it's a M-type instruction it will move MEM_ACCESS.
- ✚ Finally, the microprocessor moves to the WRITE_BACK state to store the result on Rd taking the value from memData if MemRd is 1 or from the ALUresult if its 0, then it loops back to FETCH to start the process again with the next instruction.

Operation	Opcode
A+B	0
A-B	1
A AND B	2
A OR B	3
A XOR B	4

Table 1: ALU op codes

Code:

```

1 module MCP(
2   input clk,
3   input reset,
4   output reg [2:0] current_state, // Output current state for waveform
5   output reg [2:0] next_state,    // Output next state for waveform
6   output reg [15:0] PC,           // Output PC for waveform
7   output reg [15:0] IR,           // Output Instruction Register for waveform
8   output reg [15:0] ALUresult,    // Output ALU result for waveform
9   output reg [15:0] memData,      // Output memory data for waveform
10  output reg [15:0] writeData      // Output data to be written back for waveform
11 );
12
13 // Define states for the FSM using parameters
14 parameter FETCH = 3'b000;
15 parameter DECODE = 3'b001;
16 parameter EXECUTE = 3'b010;
17 parameter MEM_ACCESS = 3'b011;
18 parameter WRITE_BACK = 3'b100;
19
20 // Control signals
21 reg RegWr, MemRd, MemWr;
22
23 // Decode signals
24 reg [3:0] opCode;
25 reg [3:0] Rd, Rs1, Rs2;
26
27 // Register File connections
28 wire [15:0] readData1, readData2;
29
30 // ALU connections
31 wire [2:0] ALUop;
32
33 // Instruction Memory Instance
34 instructionMem IM(
35   .PC(PC),
36   .instruction(instruction)
37 );
38
39

```

```

40 // Data Memory Instance
41 dataMem dm(
42     .in_data(readData2),
43     .address(Rd),
44     .clk(clk),
45     .MemRd(MemRd),
46     .MemWr(MemWr)
47 );
48
49 // Register File Instance
50 RegisterFile RF(
51     .clk(clk),
52     .read_port1(Rs1),
53     .read_port2(Rs2),
54     .write_port(Rd),
55     .writeEn(RegWr),
56     .writeData(writeData),
57     .readData1(readData1),
58     .readData2(readData2)
59 );
60
61 // Control Unit Instance
62 controlUnit CU(
63     .opCode(opCode),
64     .RegWr(RegWr),
65     .MemRd(MemRd),
66     .MemWr(MemWr),
67     .ALUop(ALUop)
68 );
69

```

```

71 // FSM State transitions
72 always @(posedge clk or negedge reset) begin
73     if (!reset)
74         current_state <= FETCH;
75     else
76         current_state <= next_state;
77 end
78
79 // FSM Control Logic: Determine next state
80 always @(*) begin
81     case (current_state)
82     FETCH: begin
83         next_state = DECODE;
84     end
85     DECODE: begin
86         if (opCode <= 4'b0100) // R-Type opcode
87             next_state = EXECUTE;
88         else if (MemRd || MemWr)
89             next_state = MEM_ACCESS;
90         else
91             next_state = FETCH;
92     end
93     EXECUTE: begin
94         if (opCode <= 4'b0100) // R-Type instruction
95             next_state = WRITE_BACK;
96         else
97             next_state = FETCH;
98     end
99     MEM_ACCESS: begin
100         if (MemRd) //load
101             next_state = WRITE_BACK;
102         else if (MemWr) //store
103             next_state = FETCH;
104         else
105             next_state = FETCH;
106     end
107     WRITE_BACK: next_state = FETCH;
108     default: next_state = FETCH;
109 endcase
110 end
111

```

```

112 // FETCH Stage
113 always @(posedge clk or negedge reset) begin
114     if (!reset)
115         begin
116             PC <= 16'b0;
117             IR <= 16'b0;
118         end
119     else if (current_state == FETCH)
120         begin
121             IR <= IM.instruction; // Fetch instruction
122             PC <= PC + 16'd2;
123         end
124     end
125
126 // DECODE Stage
127 always @(*) begin
128     if (current_state == DECODE) begin
129         opCode = IR[15:12];
130         Rd = IR[11:8];
131         Rs1 = IR[7:4];
132         Rs2 = IR[3:0];
133     end
134 end
135
136
137 // EXECUTE Stage
138 always @(*) begin
139     if (current_state == EXECUTE) begin
140         case (ALUop)
141             3'b000: ALUresult = readData1 + readData2;
142             3'b001: ALUresult = readData1 - readData2;
143             3'b010: ALUresult = readData1 & readData2;
144             3'b011: ALUresult = readData1 | readData2;
145             3'b100: ALUresult = readData1 ^ readData2;
146             default: ALUresult = 16'b0;
147         endcase
148     end
149 end
150
151 always @(posedge clk) begin
152     if (current_state == MEM_ACCESS) begin
153         if (MemRd) begin
154             memData <= dm.dataMemory[RF.register[Rs1]]; // Load data
155             $display("LOAD: Address = %h, Data = %h", RF.register[Rs1], memData);
156         end
157         if (MemWr) begin
158             dm.dataMemory[RF.register[Rs1]] <= RF.register[Rd]; // Store data
159             $display("STORE: Address = %h, Data = %h", RF.register[Rs1], RF.register[Rd]);
160         end
161     end
162 end
163
164 // WRITE-BACK Stage
165 always @(posedge clk) begin
166     if (current_state == WRITE_BACK) begin
167         if (RegWr) begin
168             if (MemRd) begin
169                 writeData <= memData; // Write loaded data to Reg[Rd]
170             end else begin
171                 writeData <= ALUresult; // Write ALU result to Reg[Rd]
172             end
173             RF.register[Rd] <= writeData; // Write-back to register
174         end
175     end
176 end
177 endmodule

```

```

297
298 //*****Instruction Memory*****//
299 module instructionMem(
300     input [15:0] PC,
301     output reg [15:0] instruction
302 );
303
304
305     reg [15:0] memory [0:255];
306
307     initial begin
308         memory[0] = 16'b0110001100100011;
309         memory[1] = 16'b0001010001100101;
310         memory[2] = 16'b0010000100110010;
311         memory[3] = 16'b0110000100100110;
312         memory[4] = 16'b0100000101100101;
313         memory[5] = 16'b0110001000110000;
314         memory[6] = 16'b0110001010000011;
315         memory[7] = 16'b0110000000100010;
316         memory[8] = 16'b0000000000101000;
317         memory[9] = 16'b0110000000110111;
318         memory[10] = 16'b0010000001000100;
319         memory[11] = 16'b0011000001010001;
320         memory[12] = 16'b0100000010001100;
321         memory[13] = 16'b0101000010010110;
322         memory[14] = 16'b0110000010100001;
323         memory[15] = 16'b0110000010110110;
324     end
325
326
327     always @ (PC) begin
328         instruction = memory[PC[7:0]];
329     end
330
331 endmodule
332
333

```

```

181
182 module RegisterFile(
183     input clk,
184     input[3:0] read_port1, read_port2, write_port,
185     input writeEn,
186     input [15:0] writeData,
187     output [15:0] readData1, readData2
188 );
189     reg [15:0] register [15:0] = '{0, 1, 2, 3, 7,
190                                     6, 4, 9, 8, 1, 5, 6, 3, 4, 6, 9};
191
192     assign readData1 = register[read_port1];
193     assign readData2 = register[read_port2];
194
195     always @(posedge clk)
196     begin
197         if(writeEn)
198             register[write_port] <= writeData;
199     end
200 endmodule
201
202
203 //*****data Memory*****//
204
205 module dataMem(
206     input [15:0] in_data,
207     input [7:0] address,
208     input clk,
209     input MemRd,
210     input MemWr
211 );
212     integer i;
213
214     reg [15:0] dataMemory [0:255];
215     initial begin
216         for(i=0; i<=255; i++)
217             dataMemory[i] = 16'b0;
218     end
219
220     always @ (posedge clk)
221     begin
222         if(MemWr)
223             dataMemory[address] <= in_data;
224     end
225 endmodule

```

```

228 //*****control Unit*****//
229 module controlUnit (
230     input [3:0] opCode,
231     output reg RegWr, MemRd, MemWr,
232     output reg [2:0] ALUop
233 );
234
235     always @(*)
236     begin
237         case(opCode)
238             4'b0000:
239                 begin
240                     RegWr = 1;
241                     MemRd = 0;
242                     MemWr = 0;
243                     ALUop = 3'b000;
244                 end
245             4'b0001:
246                 begin
247                     RegWr = 1;
248                     MemRd = 0;
249                     MemWr = 0;
250                     ALUop = 3'b001;
251                 end
252             4'b0010:
253                 begin
254                     RegWr = 1;
255                     MemRd = 0;
256                     MemWr = 0;
257                     ALUop = 3'b010;
258                 end
259             4'b0011:
260                 begin
261                     RegWr = 1;
262                     MemRd = 0;
263                     MemWr = 0;
264                     ALUop = 3'b011;
265                 end
266             4'b0100: begin
267                 RegWr = 1;
268                 MemRd = 0;
269                 MemWr = 0;
270                 ALUop = 3'b100;
271             end

```

```

252         4'b0010:
253         begin
254             RegWr = 1;
255             MemRd = 0;
256             MemWr = 0;
257             ALUop = 3'b010;
258         end
259         4'b0011:
260         begin
261             RegWr = 1;
262             MemRd = 0;
263             MemWr = 0;
264             ALUop = 3'b011;
265         end
266         4'b0100: begin
267             RegWr = 1;
268             MemRd = 0;
269             MemWr = 0;
270             ALUop = 3'b100;
271         end
272         4'b0101: begin
273             RegWr = 1;
274             MemRd = 1;
275             MemWr = 0;
276             ALUop = 3'bxxx;
277         end
278         4'b0110:
279         begin
280             RegWr = 0;
281             MemRd = 0;
282             MemWr = 1;
283             ALUop = 3'bxxx;
284         end
285         default:
286         begin
287             RegWr = 0;
288             MemRd = 0;
289             MemWr = 0;
290             ALUop = 3'b000;
291         end
292     endcase
293 end
294
295 endmodule

```

Design:

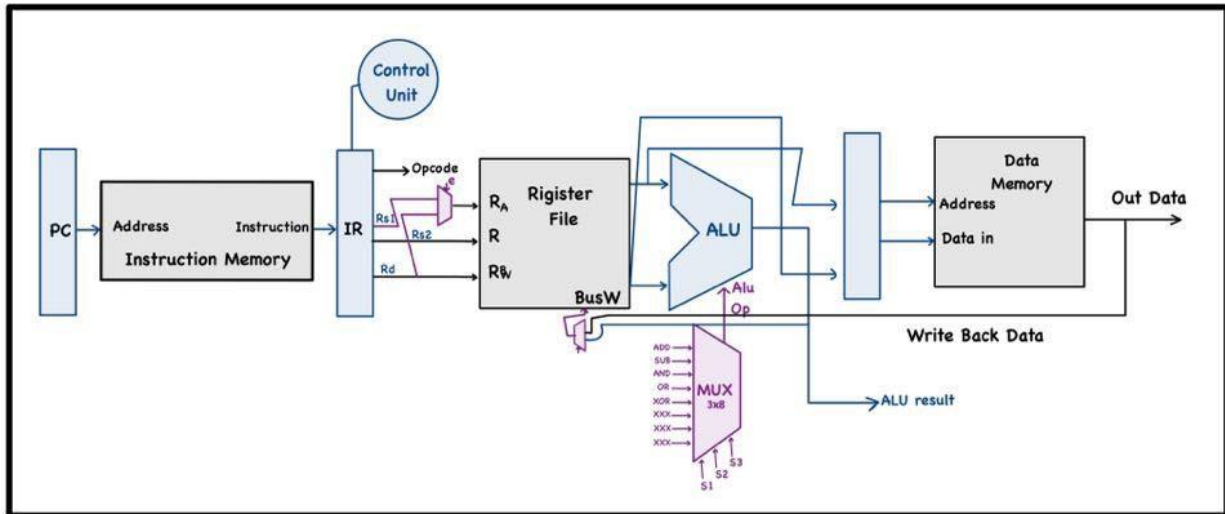


Figure 1: Design

Test cases and Simulation results

Test Bench:

```
334 //*****Test Bench*****//
335 module test_MCP;
336
337 // Inputs
338 reg clk;
339 reg reset;
340
341 // Outputs
342 wire [2:0] current_state;
343 wire [2:0] next_state;
344 wire [15:0] PC;
345 wire [15:0] IR;
346 wire [15:0] ALUresult;
347 wire [15:0] memData;
348 wire [15:0] writeData;
349
350 // Instantiate the MCP module
351 MCP uut (
352     .clk(clk),
353     .reset(reset),
354     .current_state(current_state),
355     .next_state(next_state),
356     .PC(PC),
357     .IR(IR),
358     .ALUresult(ALUresult),
359     .memData(memData),
360     .writeData(writeData)
361 );
362
363 // Clock generation
364 always #5 clk = ~clk; // 10 ns clock period
365
366 // Testbench procedure
367 initial begin
368     // Initialize inputs
369     clk = 0;
370     reset = 0;
371
372     // Apply reset
373     #10 reset = 1;
374
375
376 // Initialize data memory with test values
377 uut.dm.dataMemory[0] = 16'h0001;
378 uut.dm.dataMemory[1] = 16'h0002;
379 uut.dm.dataMemory[2] = 16'h0003;
380 uut.dm.dataMemory[3] = 16'h0004;
381 uut.dm.dataMemory[4] = 16'h0005;
382 uut.dm.dataMemory[5] = 16'h0006;
383 uut.dm.dataMemory[6] = 16'h0007;
384 uut.dm.dataMemory[7] = 16'h0008;
385 // Add more initial values if needed
386
387
388 // Populate the instruction memory with more memory operations
389 uut.IM.memory[0] = 16'b0101000100100001; // LOAD R2, [R1] (Load from address in R1)
390 uut.IM.memory[1] = 16'b0110001000110010; // STORE R3, [R2] (Store to address in R2)
391 uut.IM.memory[2] = 16'b0101001100100011; // LOAD R4, [R3] (Load from address in R3)
392 uut.IM.memory[3] = 16'b0110001100110100; // STORE R5, [R4] (Store to address in R4)
393 uut.IM.memory[4] = 16'b0101010000100101; // LOAD R6, [R5] (Load from address in R5)
394 uut.IM.memory[5] = 16'b0110010000110110; // STORE R7, [R6] (Store to address in R6)
395 uut.IM.memory[6] = 16'b0101010100100111; // LOAD R8, [R7] (Load from address in R7)
396 uut.IM.memory[7] = 16'b0110010100111000; // STORE R9, [R8] (Store to address in R8)
397
398 // Allow some time for the MCP module to execute
399 #400;
400
401 // Finish the simulation
402 $stop;
403 end
404
405 // Monitor signals for debugging
406 initial begin
407     $monitor("Time: %0d | State: %b | PC: %h | IR: %h | ALUresult: %h | memData: %h | writeData: %h",
408             $time, current_state, PC, IR, ALUresult, memData, writeData);
409 end
410
411 endmodule
```

Figure 2: Test Bench

Results:

```

# Console
# run
# # KERNEL: Time: 0 | State: 000 | PC: 0000 | IR: 0000 | ALResult: xxxx | memData: xxxx | writeData: xxxx
# # KERNEL: Time: 15 | State: 001 | PC: 0002 | IR: 6323 | ALResult: xxxx | memData: xxxx | writeData: xxxx
# # KERNEL: Time: 25 | State: 011 | PC: 0002 | IR: 6323 | ALResult: xxxx | memData: xxxx | writeData: xxxx
# # KERNEL: STORE: Address = 0004, Data = 0003
# # KERNEL: Time: 35 | State: 000 | PC: 0002 | IR: 6323 | ALResult: xxxx | memData: xxxx | writeData: xxxx
# # KERNEL: Time: 45 | State: 001 | PC: 0004 | IR: 5323 | ALResult: xxxx | memData: xxxx | writeData: xxxx
# # KERNEL: Time: 55 | State: 011 | PC: 0004 | IR: 5323 | ALResult: xxxx | memData: xxxx | writeData: xxxx
# # KERNEL: LOAD: Address = 0004, Data = xxxx
# # KERNEL: Time: 65 | State: 100 | PC: 0004 | IR: 5323 | ALResult: xxxx | memData: 0003 | writeData: xxxx
# # KERNEL: Time: 75 | State: 000 | PC: 0004 | IR: 5323 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: Time: 85 | State: 100 | PC: 0006 | IR: 5425 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: Time: 95 | State: 011 | PC: 0006 | IR: 5425 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: LOAD: Address = 0004, Data = 0003
# # KERNEL: Time: 105 | State: 100 | PC: 0006 | IR: 5425 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: Time: 115 | State: 000 | PC: 0006 | IR: 5425 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: Time: 125 | State: 001 | PC: 0008 | IR: 5527 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: Time: 135 | State: 011 | PC: 0008 | IR: 5527 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: LOAD: Address = 0004, Data = 0003
# # KERNEL: Time: 145 | State: 000 | PC: 0008 | IR: 5527 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: Time: 155 | State: 000 | PC: 0008 | IR: 5527 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: Time: 165 | State: 001 | PC: 000A | IR: 0028 | ALResult: xxxx | memData: 0003 | writeData: 0003
# # KERNEL: Time: 175 | State: 010 | PC: 000A | IR: 0028 | ALResult: 000d | memData: 0003 | writeData: 000d
# # KERNEL: Time: 185 | State: 100 | PC: 000A | IR: 0028 | ALResult: 000d | memData: 0003 | writeData: 000d
# # KERNEL: Time: 195 | State: 000 | PC: 000A | IR: 0028 | ALResult: 000d | memData: 0003 | writeData: 000d
# # KERNEL: Time: 205 | State: 001 | PC: 000C | IR: 2044 | ALResult: 000d | memData: 0003 | writeData: 000d
# # KERNEL: Time: 215 | State: 010 | PC: 000C | IR: 2044 | ALResult: 0003 | memData: 0003 | writeData: 000d
# # KERNEL: Time: 225 | State: 100 | PC: 000C | IR: 2044 | ALResult: 0003 | memData: 0003 | writeData: 000d
# # KERNEL: Time: 235 | State: 000 | PC: 000C | IR: 2044 | ALResult: 0003 | memData: 0003 | writeData: 0003
# # KERNEL: Time: 245 | State: 010 | PC: 000C | IR: 408C | ALResult: 0003 | memData: 0003 | writeData: 0003
# # KERNEL: Time: 255 | State: 010 | PC: 000C | IR: 408C | ALResult: 000A | memData: 0003 | writeData: 0003
# # KERNEL: Time: 265 | State: 100 | PC: 000E | IR: 408C | ALResult: 000A | memData: 0003 | writeData: 0003
# # KERNEL: Time: 275 | State: 000 | PC: 000E | IR: 408C | ALResult: 000A | memData: 0003 | writeData: 000A
# # KERNEL: Time: 285 | State: 001 | PC: 0010 | IR: 60A1 | ALResult: 000A | memData: 0003 | writeData: 000A
# # KERNEL: Time: 295 | State: 011 | PC: 0010 | IR: 60A1 | ALResult: 000A | memData: 0003 | writeData: 000A
> restart

```

```
# # KERNEL: STORE: Address = 0006, Data = 000a
# # KERNEL: Time: 305 | State: 000 | PC: 0010 | IR: 60a1 | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 315 | State: 001 | PC: 0012 | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 325 | State: 000 | PC: 0012 | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 335 | State: 001 | PC: 0014 | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 345 | State: 000 | PC: 0014 | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 355 | State: 001 | PC: 0016 | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 365 | State: 000 | PC: 0016 | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 375 | State: 001 | PC: 0018 | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 385 | State: 000 | PC: 0018 | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 395 | State: 001 | PC: 001a | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # KERNEL: Time: 405 | State: 000 | PC: 001a | IR: xxxx | ALUresult: 000a | memData: 0003 | writeData: 000a
# # RUNTIME: Info: RUNTIME 0070 MCP.v (402): $stop called.
```

 


Figure 3: Results

Initially the pc starts at 0 and the IR stores the instruction in the 0 address which is 6323 and stores the value of R3 which is 3 on the data memory with as address of 4 since this is value loaded into R1 and as shown in the wave form the processor has successfully done this instruction since writeData is 3 which is the data will be written back on the memory.

Then, when pc is 2 the IR is 5323 which is supposed to load the value of memory[4] since 4 is the value inside R2, now the value of memory[4] is 3 since this is what we stored in it in the previous instruction so the memData should be 3 which is correct as shown in the wave form.

The results in ALU operations are correctly performed note that when the pc is 8 the IR is 0028 (with a bit of delay) which is the value we initially stored in the instruction memory this instruction is ADD R0 R2 R8 and the values in R2, R8 are 4,9 respectively so the ALUresult is expected to be 10 which is true and the result was successfully loaded into the writeData to be loaded into the result register (Rd), proving the ability of the processor in performing arithmetic operations.

The remaining instructions are handled similarly, proving the efficiency of the processor.

Conclusion and future work

In this project, we successfully designed and verified a multi-cycle processor that proved its ability of handling instructions over several clock cycles. The design was implemented using Verilog designing multiple modules such as Memory, Data path, Control unit and a top module combining them all, each stage functioned correctly from FETCH to WRITE-BACK ensuring correct execution. For future improvements, the processor could be improved by adding additional ALU operations for wider arithmetic functions, as well as providing conditional instructions such as jump and branch. These improvements would increase the processor's capability to handle complex tasks and increase its efficiency and adaptability for more varied tasks.